
Subject: RIAA preamp project

Posted by [FL152](#) on Fri, 22 Apr 2011 16:26:26 GMT

[View Forum Message](#) <> [Reply to Message](#)

It started six years ago on this forum, with some talk about RIAA preamps, and I offered an idea of simple, two E188CC tubes based, direct coupled design. Passive RC RIAA filter between the gain stages. Well, nobody built it, including me, years went by, and besides some experiments with similar D3a / C3g design, I almost forgot it. And yes, I was out of the forums for the last five years. It restarted this Christmas, when Santa brought me the new Rega RP-1 turntable. Its Ortofon OM-5E MM cartridge puts 4 mV output on 47 k / 200-600 pF load. The sensitivity of my 300B SET is 1,2 Vrms / 25 kOhms, and that means some requirements for the RIAA preamp:

- amplification 300 times on 1 kHz (~50 dB)
- input capacitance isn't too critical, but better to be on the lower side, ~200 pF
- low output impedance, < 1 kOhms, to drive about 3 m of cables and 25 k power amp input

And I put some additional requirements:

- low RIAA error, <0,5 dB
- simple, direct, good sounding, polarity (phase) non-inverting, two tubes per channel design
- large overload margin on all frequencies (~35 dB, by M. Jones)
- use of the „normal" parts, that I have or can easily obtain
- compact design, stand alone unit that can „drive" power amp to the full output

When I searched my parts collection I actually found everything I need - enclosure from salvaged '50s cinema console amplifier, two DN2540N5 based CCS modules I built for some other project and forgot about it, two MJE350/BC558/LED CCS modules I built years ago too, some quality NOS ERO KP1836 capacitors, even one multi-secondary small toroid PT I used for experiments, four noval teflon sockets...plus many other parts.

A quick calculation I made on the back of an envelope gave me the RIAA filter values. This time I decided to use low impedance version, smaller Rs, and bigger Cs. This is arranged with the parts I actually have, but can be easily changed for different RC values with formulas and schematic of passive RIAA filter.

Here's the complete schematic, one channel shown:

And there's a CCS schematic, known from old projects:

Actually, Ra consists of a series Rout from the first tube (D3a in triode), R4=15 k and Rx in series, in parallel with Rg=R6 from 2nd stage, trioded E180F. We must know the Rout~rp value of D3a, and a little experiment is in the order. I measured the amplification of the first stage alone, with

CCS, this gives me $A=70 \sim \mu$.

Then I substituted CCS with resistive anode load, with a chosen value that gives me the same OP. I used $B+ = 305 \text{ V}$, and with LED bias $U_k = 1,82 \text{ V}$ anode voltage was $U_a = 145 \text{ V}$. CCS was set to 11 mA, and then $R_I = 15 \text{ k}\Omega$ was chosen. It gives almost the same OP, but measured amplification was lower, 56,6 times, because this time r_p of the tube and R_I formed a resistive divider, $A = (\mu \times R_I) / (r_p + R_I)$. With a little math help, we can rearrange the formula and get $r_p = (\mu \times R_I / A) - R_I = (70 \times 15 / 56,6) - 15 = 3,56 \text{ k}\Omega$.

This value is larger than theoretical, couple of Ohms of unbypassed resistance of the LED multiplied with tube μ rises the value of tubes r_p .

R_x is used in addition with $R_4 = 15 \text{ k}$, to „fine tune“ the final R_a with the actual measured value of r_p . It's a best for the potential builder to check the r_p of the actual tubes in OP he chooses. Larger current values through V_1 gives lower r_p and somewhat lower noise, but I chose 11 mA for two reasons longevity, and sound. IME, high S tubes tend to sound „strident“ a bit, less so with lower currents.

I used normal, anode out from the first stage, because of its sound. This gives the $R_a : r_p$ ratio about four, then r_p is the significant part of the series RIAA resistor, R_a . But, IME, fear not, D3a is 10000 h SQ tube, and besides, changes in S (together with changes in r_p) in say +/- 10%, change the RIAA characteristics very little. Someone can always try low impedance μ -out on the V_1 , too - then use R_x about 3k3 (and find exact R_{out} of the μ -out by measurements).

PS is passive, with parts I have at hand and can physically fit in the chassis. Theoretically, after all that CLCLCRC filtering, and large PSRR from CCSs, we cannot „hear“ the PS.

But, practically, rectifier changes / types are sonically present. $B+$ isn't critical, everything from 250V - 350V would work, but I preferred lower values because of the heat dissipation in CCS heat sinks.

Full PS Schematic is in the "Projects" files.

By listening tests, RCA 5V4G nicely fits between Mullard E180F, and AEG gray anode D3a (probably Siemens, too). Some selection between various D3a for low microphonics and noise is beneficial here.

Here's a photo of the finished and working preamp. I used an old chassis, and reused old holes...for the ugly large holes between the tubes I actually used 10 mm red LEDs. They look funny, and give a bit more voltage (and light) than their 5 mm brothers, about 1,82V with 11 mA.

And here's an inside view, this is my version of compact unit and „old school“ microelectronics. It looks like Frankenstein's cell phone, actually...

There are six PCBs inside, four of them are CCS modules, PCBs are my design, but someone can always use the kits. We have capacitors PCB (those ERO caps are radial), and heater regulator PCB, mounted on L sized heat sink.

I don't have pro-measuring devices, and I used what I have (oscilloscope, multimeter, test CD). The results are good:

-with D3a/E180F combination, I measured A=292 times on 1 kHz, over 400 times with D3a/D3a...but sonically I preferred the former set a bit.
-the frequency response was tough to measure with my equipment, but if we can trust it, we have a nice flat response (0,1...0,2 dB deviation) through 50 - 500 Hz, with a gentle rise to the final 0,46 dB on 20 kHz.
-noise level is very low, with normal listening level you can hear it a bit with your ear close to the twitter.
-overload margin is very good too (>33 dB or better on all frequencies, 20Hz-20 kHz)), you can put out over 100 Vpp from this preamp with ease, and this can be heard!

Subjective, after a few tens of hours of burn-in, tubes rolling, other little changes and experiments, I'm very pleased with the sound - open, dynamic, powerfull, clean, „fits" good with my SET, and now I'm listening LPs I didn't listen to for decades. And I'm actually surprised with the excellent sound that many of these LPs have!

Be carefull about grounding and placing the components. I simply used local star grounds on each tube socket, and then one and only (star) ground on the chasis, close to the inputs. Total amplification on 50 Hz is about 2000x , and if we have only 10 uV of 50Hz mains hum induced somehow on the input, that means 20 mV on the output, or only 35 dB below nominal output.

This is a short version (haha) of this practical design. Unfortunately, I don't have enough time for details...but with a bit of DIY experience those little pieces of RIAA puzzle can be solved by potential builder.

All in all, I wanted to share this project with old forum...enjoy!

File Attachments

- 1) [RIAA calc.bmp](#), downloaded 37402 times
 - 2) [RIAA pre.bmp](#), downloaded 40785 times
 - 3) [CCS.bmp](#), downloaded 37608 times
 - 4) [RIAA preamp.jpg](#), downloaded 36734 times
 - 5) [IMG_0385.jpg](#), downloaded 35783 times
-

Subject: Re: RIAA preamp project
Posted by [Wayne Parham](#) on Fri, 22 Apr 2011 18:50:30 GMT
[View Forum Message](#) <> [Reply to Message](#)

Very good to see you here again, Damir. You've been sorely missed. Now, to roll up my sleeves and study this project you've written about...

Subject: Re: RIAA preamp project
Posted by [gofar99](#) on Tue, 26 Apr 2011 16:15:00 GMT
[View Forum Message](#) <> [Reply to Message](#)

Hi, A lot of thought went into the project . I have been working for about 8 months or so on a RIAA preamp. I tried several variations and none have quite done what I want. I have no problem with gain, overload, Z out, frequency response. The one area I want is a S/N of over 90 dbv at 1 volt output. I can get 85 now. The best topology so far is a 12AX7 SRPP feeding a second 12AX7 SRPP followed by a E88CC cathode follower. The equalization is active between the third and first stage. The active mode gave better S/N than a passive one between the first and second stages. I sympathize with the problems you have experienced with measurements. I have a raft of test gear incl 2 DSO, a HP distortion analyzer, two signal generators and more meters than I can count. Still the process of measuring RIAA preamps is both tedious and can be misleading. When I get it a little closer to what I want, I'll post it.

Where did you get the power transformer? Small ones for this type of project are difficult to locate except through overseas sources.

Subject: Re: RIAA preamp project
Posted by [Wayne Parham](#) on Tue, 26 Apr 2011 18:17:30 GMT
[View Forum Message](#) <> [Reply to Message](#)

Damir lives in Croatia, so he has no trouble with the overseas part.

As for us stateside, have you ever tried Heyboer? We've had them do some custom winds for projects in this forum, and the prices were very reasonable, even in relatively low quantities.

Subject: Re: RIAA preamp project
Posted by [FL152](#) on Tue, 26 Apr 2011 18:34:31 GMT
[View Forum Message](#) <> [Reply to Message](#)

Hello, "Antek" sells small toroids, now even with electrostatic shields. I didn't try them so far, but the price seems reasonable. In this project I didn't use anything exotic, I have another project right now (microphone preamp) with "AE-Europe" duple C-core power transformer. Did you try other tubes / topologies for the first stage? I know that is an "interactive" job, but 6072/12AY7 comes to my mind...as D3a and E810F...

Subject: Re: RIAA preamp project
Posted by [gofar99](#) on Tue, 26 Apr 2011 20:01:59 GMT

[View Forum Message](#) <> [Reply to Message](#)

Hi, I'll check out the Heyboer ones. Antek Trannies are fine, just huge. I did use one on the RIAA preamp with the metal shield. It looked a lot like the civil war ship monitor. Worked, just about 10 pounds of iron to deliver 50ma. Good prices though. You need to watch the wiring on some as they are all not labeled or color coded the same - even with the same part number.

Subject: Re: RIAA preamp project
Posted by [gofar99](#) on Sun, 17 Jul 2011 02:19:37 GMT
[View Forum Message](#) <> [Reply to Message](#)

Hi, I don't want to hijack the thread, but I posted my latest iteration of the phono preamp I've been working on under the thermionic projects with a few updates on my company sponsored section. I want to thank Damir and a few others for their insights and comments on that project. RIAA preamps seem at first glance to be simple devices. This is not the case. All designs have to juggle, response, distortion and signal to noise effectively and at the same if a diy version is planned, find components that are easy to obtain for other builders. There is considerably reduced value to a project that uses parts no one can get. Warm up your soldering irons and build something...

Subject: Re: RIAA preamp project
Posted by [FL152](#) on Sun, 17 Jul 2011 12:32:09 GMT
[View Forum Message](#) <> [Reply to Message](#)

Morgan Jones: "It is difficult to design a pre-amplifier of acceptable noise and overload capability using this network („all in one go" equalization), so this topology can usually be excluded." Because of this, he used „split EQ" technique, and 3-4 stages preamps. IMO/IME, it's not that hard to build a quality 2-stage preamp with passive EQ in between, if we respect some basic things. One of the basics is that we must include output resistance of the 1st stage, as well as input capacitance of both stages into consideration. Ideally, output resistance of the 1st stage „feeding" RIAA EQ must have a very small impedance, at least this impedance must be a small part of the series RIAA resistor. In this case, variations between tubes and change in S/rp during work have a minimal impact on the RIAA accuracy, and „sound" of our preamp. It's a designer's „duty" to find workable combinations of tubes/topologies and RIAA RC values...and to check that in practice. Similarly, input capacitance of the 2nd stage (Miller!) is a part of the parallel capacitor in RIAA network. Unfortunately, usually we can't expect those RC values to „fit" into standard values available, and series / parallel combinations of resistors and capacitors are often a necessity...plus measuring its real values with good instruments.

Subject: Re: RIAA preamp project

Posted by [gofar99](#) on Sun, 17 Jul 2011 22:18:15 GMT

[View Forum Message](#) <> [Reply to Message](#)

Hi, I read the book too and while there are good points, it is not impossible. However, I have something I want to try. Following the SRPP input stage with a cathode follower to feed the network. It would look similar to the output stage. It would provide a low impedance drive to the network and eliminate many of the shortcomings of a high gain first stage. Good thoughts, I suspect that trying to get a really good phono preamp has driven more than a few diyers crazy. Maybe that is why there are so many simple ones. It probably accounts for why many of the name brand ones now are IC based.

Subject: Re: RIAA preamp project

Posted by [gofar99](#) on Sat, 08 Jun 2013 03:29:28 GMT

[View Forum Message](#) <> [Reply to Message](#)

Hi, I recently found a good way to test phono preamps. You need to build a reverse RIAA filter (not too difficult and only about 6 parts) and then the way I do it is use a DSO that has a built in signal generator and can do direct Bode plots of the results. With a good RIAA inverse filter the result should be a straight line. Mine is accordingly within +/- 0.2 db from 20HZ to just past 22KHZ. Ruler flat in the 100-10K range. The S/N is right on - 89dbv with common JJ ECC803S and ECC81S tubes. Low noise ones can bring it down about another 3 db. I stuck with the passive filtering as it seemed to sound better. Hard to define how, just better.

BTW you are quite correct that good grounding is extremely important. Layout is equally important. This is the type of project that can not be just thrown together and expected to work well.
